

Charge Amplifiers Noise Analysis Report

Matteo Polo

December 14, 2023

Contents

1	Cremat Cr-110 + Cr-150	2
2	Amptek A250	3
3	Pulse Generator Only	4
4	Conclusions	5

1 Cremat Cr-110 + Cr-150

- Test input: Used Agilent pulse generator. Square wave with amplitude $V_{pp} = [140-180]\text{mV}$. Frequency 1kHz. $Q_{in} = V_{pp} * C2 = V_{pp} * 1\text{pF}$.
- Parameters set on CAEN 5780:

Record length	$40\mu s$
Polarity	neg
Coarse gain	x16
Trap raise time	$5\mu s$
Trap flat top	$5\mu s$
Trap pole zero	$130\mu s$
Peaking time	50 %
N sample peak	64



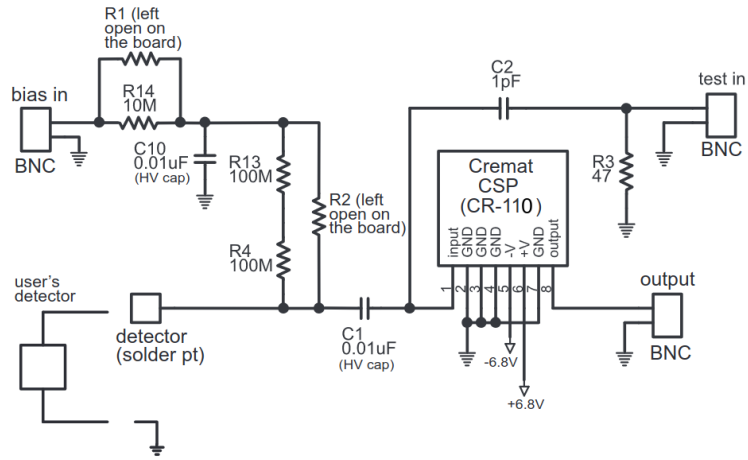


Figure 1: Cr-110 + Cr-150 Circuit

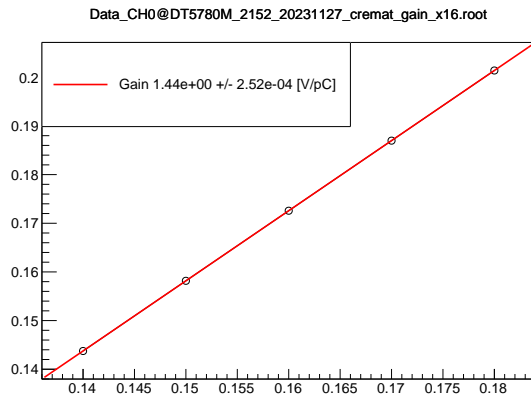

(a) Gain

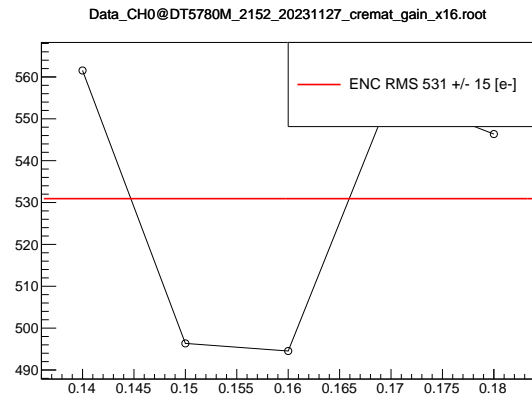

(b) Noise

Figure 2: Figure

2 Amptek A250

- Test input: Used Agilent pulse generator. Square wave with amplitude $V_{pp} = [140-180]\text{mV}$. Frequency 1kHz. $Q_{in} = V_{pp} * C2 = V_{pp} * 1\text{pF}$.
- Parameters set on CAEN 5780:

Record length	$20\mu\text{s}$
Polarity	neg
Coarse gain	x16
Trap raise time	$0.5\mu\text{s}$
Trap flat top	$0.3\mu\text{s}$
Trap pole zero	$1\mu\text{s}$
Peaking time	50 %
N sample peak	16

- To reduce the output offset, which is 600mV, a capacitance of 100pF was added in parallel to a resistor of $3\text{M}\Omega$.



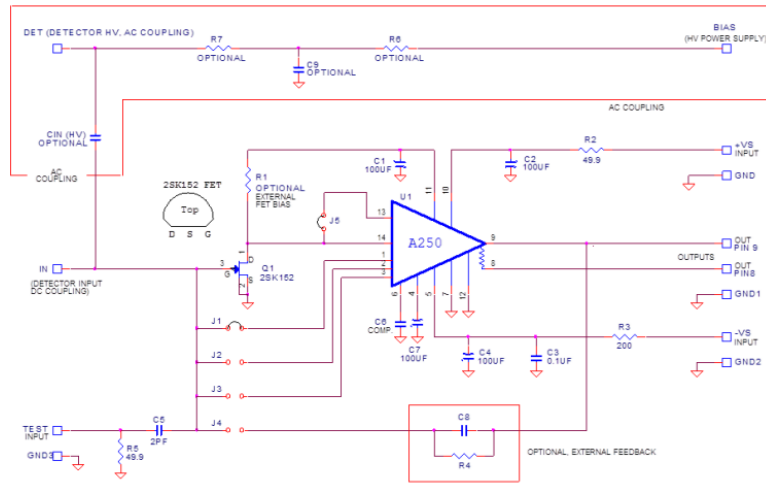


Figure 3: A250 + PC250 Circuit

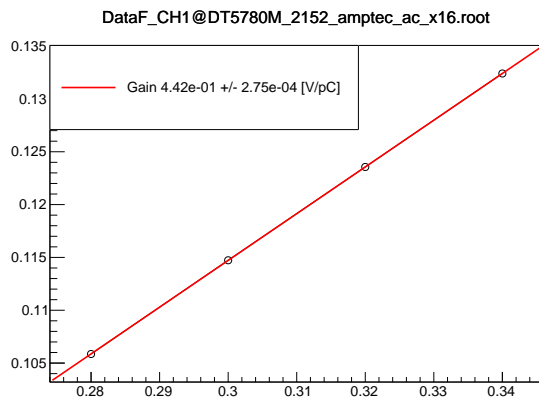

(a) Gain

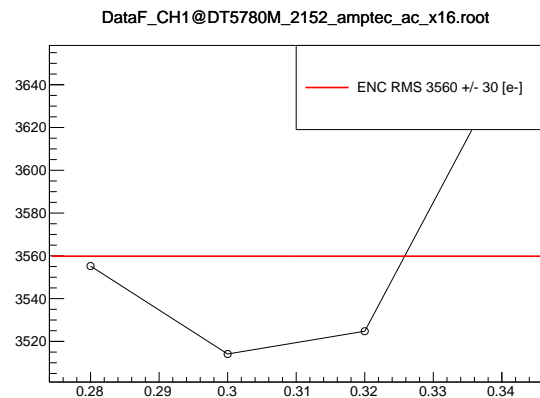

(b) Noise

Figure 4: Figure

3 Pulse Generator Only

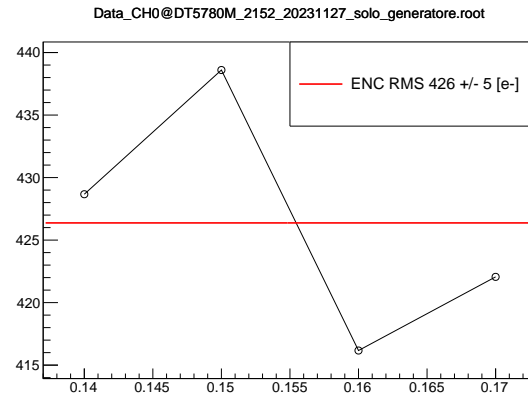


Figure 5: Noise

4 Conclusions

The following formula was used for noise calculation, to remove the noise contribution from the pulser in the amplifier + pulser system.

$$ENC_{amp} = \sqrt{ENC_{amp+pul}^2 - ENC_{pul}^2} \quad (1)$$

Amplifier	Equivalent noise charge
Cremat Cr-110	$316 \pm 5 \text{ e}^-$
Amptek A250	$3534 \pm 5 \text{ e}^-$

Table 1: Final Results CR-150